

# LAB 1

**OBJECTIVE:** To design and simulate a 2-input AND gate using VHDL, and verify its functionality using a testbench.

## TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

## THEORY:

The aim of this lab is to create a simple 2-input AND gate in VHDL and simulate it using a testbench. The design code describes the logic of the AND gate, and the testbench applies all possible input combinations to validate the behavior of the gate.

## VHDL CODE

### DESIGN:

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity andgate is
    port( a,b:in std_logic;
          c: out std_logic);
end andgate;
```

```
architecture behavior of andgate is
    begin
        c <= a and b;
    end behavior;
```

### TESTBENCH

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity andgate_tb is
    ---> no content
end andgate_tb;
```

```
architecture test of andgate_tb is
    component andgate
        port(a,b: in std_logic;
```

```
          c: out std_logic);
    end component;

    signal ak,bk,ck: std_logic;

    begin

        and_gate: andgate port map(a=>ak,
        b=>bk, c=>ck);

        process begin

            ak <= '0';bk <= '0';wait for 1 ns;


            ak <= '0';bk <= '1';wait for 1 ns;

            ak <= '1';bk <= '0';wait for 1 ns;

            ak <= '1';bk <= '1';wait for 1 ns;

            assert false report "Completed
            successfully";
            wait;
        end process;
    end test;
```

### Output:

 

## CONCLUSION:

The 2-input AND gate was successfully simulated. The output matched the expected truth table for all input combinations. The use of a simple testbench allowed for effective verification of the circuit behavior in a VHDL simulation environment.