

**Tribhuvan University
Institute Of Science and Technology**


Prithvi Narayan Campus

BSc.CSIT Program



PRACTICAL REPORT

(Computer Architecture)

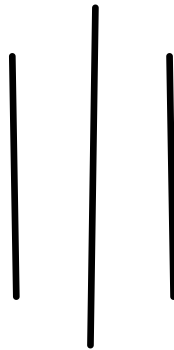

Submitted To

Mrs. Amrita Thapa

Department of Computer Science & Information Technology
Prithvi Narayan Campus, Pokhara

Submitted By

Mahesh Kumar Udas

Roll No. 21

2080 Batch

2nd Year / 3rd Semester

INDEX

Name: Mahesh Kumar Udas

Roll No.: 21

Faculty: BSc.CSIT

Semester: Third

Subject: Computer Architecture

Year : Second

S.N.	Title	Date of Submission	Sign
1.	To design and simulate a 2-input AND gate using VHDL, and verify its functionality using a testbench.	2081/12/	
2.	To design and simulate a 2-input OR gate using VHDL, and verify its functionality using a testbench.	2081/12/	
3.	To design and simulate a NOT gate using VHDL, and verify its functionality using a testbench.	2081/12/	
4.	To design and simulate a NAND gate using VHDL, and verify its functionality using a testbench.	2081/12/	
5.	To design and simulate a Half Adder Circuit using VHDL, and verify its functionality using a testbench.	2081/12/	
6.	To design and simulate a Full Adder Circuit using VHDL, and verify its functionality using a testbench.	2081/12/	

LAB 1

OBJECTIVE: To design and simulate a 2-input AND gate using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

The aim of this lab is to create a simple 2-input AND gate in VHDL and simulate it using a testbench. The design code describes the logic of the AND gate, and the testbench applies all possible input combinations to validate the behavior of the gate.

VHDL CODE

DESIGN:

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity andgate is  
  port( a,b:in std_logic;  
        c: out std_logic);  
end andgate;
```

```
architecture behavior of andgate is  
  begin  
    c <= a and b;  
end behavior;
```

TESTBENCH


```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity andgate_tb is  
  ---> no content  
end andgate_tb;
```

```
architecture test of andgate_tb is  
  component andgate  
    port(a,b: in std_logic;
```

```
        c: out std_logic);  
  end component;  
  
  signal ak,bk,ck: std_logic;  
  
  begin  
  
    and_gate: andgate port map(a=>ak,  
                               b=>bk, c=>ck);  
  
    process begin  
  
      ak <= '0';bk <= '0';wait for 1 ns;  
  
      ak <= '0';bk <= '1';wait for 1 ns;  
  
      ak <= '1';bk <= '0';wait for 1 ns;  
  
      ak <= '1';bk <= '1';wait for 1 ns;  
  
      assert false report "Completed  
successfully";  
      wait;  
    end process;  
  end test;
```

Output:

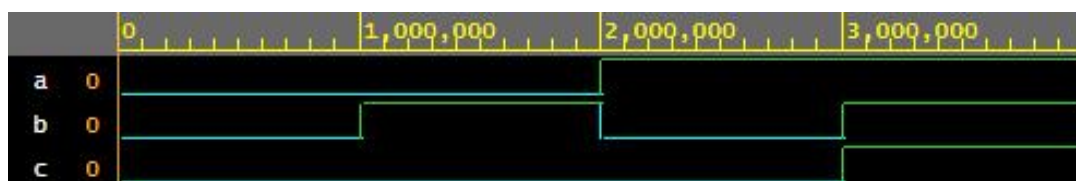

CONCLUSION:

The 2-input AND gate was successfully simulated. The output matched the expected truth table for all input combinations. The use of a simple testbench allowed for effective verification of the circuit behavior in a VHDL simulation environment.

LAB 2

OBJECTIVE: To design and simulate a 2-input OR gate using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

The aim of this lab is to create a simple 2-input OR gate in VHDL and simulate it using a testbench. The design code describes the logic of the OR gate, and the testbench applies all possible input combinations to validate the behavior of the gate.

VHDL CODE

DESIGN:

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity orgate is  
  port( a,b:in std_logic;  
        c: out std_logic);  
end orgate;
```

```
architecture behavior of orgate is  
  begin  
    c <= a or b;  
end behavior;
```

TESTBENCH


```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity orgate_tb is  
  ---> no content  
end orgate_tb;
```

```
architecture test of orgate_tb is  
  component orgate  
    port(a,b: in std_logic;
```

```
        c: out std_logic);  
  end component;  
  
  signal ak,bk,ck: std_logic;  
  
  begin  
  
    and_gate: orgate port map(a=>ak,  
                              b=>bk, c=>ck);  
  
    process begin  
  
      ak <= '0';bk <= '0';wait for 1 ns;  
  
      ak <= '0';bk <= '1';wait for 1 ns;  
  
      ak <= '1';bk <= '0';wait for 1 ns;  
  
      ak <= '1';bk <= '1';wait for 1 ns;  
  
      assert false report "Completed  
successfully";  
      wait;  
    end process;  
  end test;
```

Output:

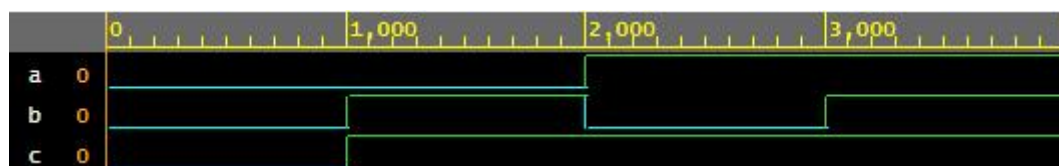

CONCLUSION:

The 2-input OR gate was successfully simulated. The output matched the expected truth table for all input combinations. The use of a simple testbench allowed for effective verification of the circuit behavior in a VHDL simulation environment.

LAB 3

OBJECTIVE: To design and simulate a NOT gate using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

The aim of this lab is to create a NOT gate in VHDL and simulate it using a testbench. The design code describes the logic of the NOT gate, and the testbench applies both possible input combinations to validate the behavior of the gate.

VHDL CODE

DESIGN:

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity notgate is  
  port( a: in std_logic;  
        c: out std_logic);  
end andgate;
```

```
architecture behavior of notgate is  
  begin  
    c <= not a;  
end behavior;
```

TESTBENCH

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity notgate_tb is  
  ---> no content  
end notgate_tb;
```


```
architecture test of notgate_tb is  
  component notgate  
    port(a: in std_logic;  
          c: out std_logic);  
  end component;
```

```
  signal ak,ck: std_logic;  
  
  begin  
  
    and_gate: notgate port map(a=>ak,c=>ck);  
  
    process begin
```

```
      ak <= '0'; wait for 1 ns;  
      ak <= '1'; wait for 1 ns;
```

```
      assert false report "Completed  
successfully";  
      wait;  
    end process;  
  end test;
```

Output:

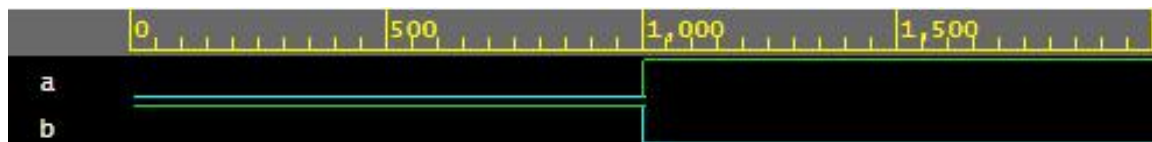

CONCLUSION:

The NOT gate was successfully simulated. The output matched the expected behavior where ck is the inverse of ak for all input combinations. The use of a simple testbench allowed for effective verification of the circuit behavior in a VHDL simulation environment.

LAB 4

OBJECTIVE: To design and simulate a NAND gate using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

The aim of this lab is to create a NAND gate in VHDL and simulate it using a testbench. The design code describes the logic of the NAND gate, and the testbench applies both possible input combinations to validate the behavior of the gate.

VHDL CODE

DESIGN

```
library ieee;
use ieee.std_logic_1164.all;

entity nandgate is
    port(
        a,b:in std_logic;
        c: out std_logic
    );
end nandgate;
```

```
architecture behavior of nandgate is
    begin
        c <= not (a and b);
    end behavior;
```

TESTBENCH

```
library ieee;
use ieee.std_logic_1164.all;

entity nandgate_testbench is
end nandgate_testbench;

architecture test of nandgate_testbench is
    component nandgate
```

```
    port(
        a,b: in std_logic;
        c: out std_logic
    );
end component;

    signal ak,bk,ck: std_logic;

    begin


        nand_gate: nandgate port map(a=>ak,
        b=>bk, c=>ck);

        process begin

            ak <= '0';bk <= '0';wait for 1 ns;
            ak <= '0';bk <= '1';wait for 1 ns;
            ak <= '1';bk <= '0';wait for 1 ns;
            ak <= '1';bk <= '1';wait for 1 ns;

            assert false report "Completed
            successfully";
            wait;
        end process;
    end test;
```

Output:

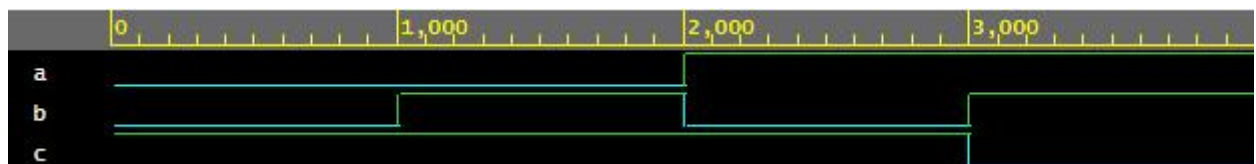

CONCLUSION:

The NOT gate was successfully simulated. The output matched the expected behavior where ck is the inverse of ak for all input combinations. The use of a simple testbench allowed for effective verification of the circuit behavior in a VHDL simulation environment.

LAB 5

OBJECTIVE: To design and simulate a **Half Adder Circuit** using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

A Half Adder is a basic combinational circuit that adds two single-bit binary numbers. It produces two outputs:

- Sum (S): XOR of inputs A and B
- Carry (C): AND of inputs A and B

VHDL CODE

DESIGN

```
library ieee;
use ieee.std_logic_1164.all;

entity ha is
    port(
        a: in std_logic;
        b: in std_logic;
        c: out std_logic;
        s: out std_logic);
end ha;
```

```
architecture behave of ha is
begin
    s <= a xor b;
    c <= a and b;
end behave;
```

TESTBENCH

```
library ieee;
use ieee.std_logic_1164.all;

entity ha_testbench is
end ha_testbench;
```

```
architecture test of ha_testbench is
    component ha
        port(a: in std_logic;
             b: in std_logic;
             c: out std_logic;
             s: out std_logic);
    end component;


    signal ain, bin, carry, sum : std_logic;

begin
    half_adder: ha port map (a => ain, b =>
        bin, c => carry, s => sum);

    process begin
        ain <= '0'; bin <= '0'; wait for 1 ns;
        ain <= '0'; bin <= '1'; wait for 1 ns;
        ain <= '1'; bin <= '0'; wait for 1 ns;
        ain <= '1'; bin <= '1'; wait for 1 ns;

        assert false report "Reached end of test";wait;
    end process;
end test;
```

Output:

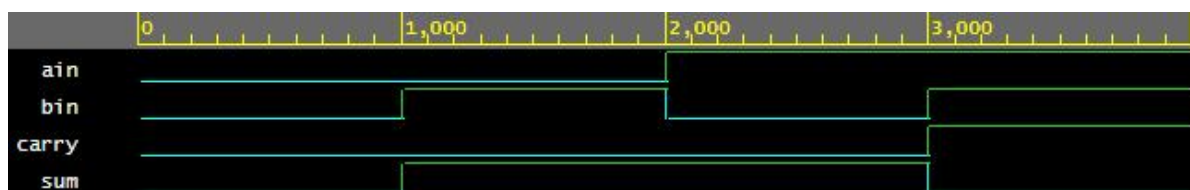

CONCLUSION:

The Half Adder was successfully implemented and simulated in VHDL. The outputs of the simulation matched the expected values based on the truth table of a half adder. The testbench applied all input combinations and validated the behavior effectively.

LAB 6

OBJECTIVE: To design and simulate a **Full Adder Circuit** using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

A Full Adder adds three one-bit binary numbers (A, B, and Carry-in) and outputs a Sum and a Carry-out. It performs the function:

- Sum (S) = A XOR B XOR Cin
- Carry-out (Cout) = (A XOR B) AND Cin OR (A AND B)

VHDL CODE

DESIGN

```
library ieee;
use ieee.std_logic_1164.all;

entity fa is
    port(
        a: in std_ulogic;
        b: in std_ulogic;
        cin: in std_ulogic;
        cout: out std_ulogic;
        s: out std_ulogic
    );
end fa;

architecture behave of fa is
begin
    s <= (a xor b) xor cin;
    cout <= ((a xor b) and cin) or (a and b);
end behave;

-- Full Adder Component
cout: out std_ulogic;
s: out std_ulogic;


);
end component;

signal ain, bin, cin, cout, sum : std_logic;

begin
    full_adder: fa port map (a => ain,
        b => bin, cin => cin, cout => cout, s => sum);

    process begin
        ain <= '0'; bin <= '0'; cin <= '0'; wait for 1 ns;
        ain <= '0'; bin <= '0'; cin <= '1'; wait for 1 ns;
        ain <= '0'; bin <= '1'; cin <= '0'; wait for 1 ns;
        ain <= '0'; bin <= '1'; cin <= '1'; wait for 1 ns;
        ain <= '1'; bin <= '0'; cin <= '0'; wait for 1 ns;
        ain <= '1'; bin <= '0'; cin <= '1'; wait for 1 ns;
        ain <= '1'; bin <= '1'; cin <= '0'; wait for 1 ns;
        ain <= '1'; bin <= '1'; cin <= '1'; wait for 1 ns;
        assert false report "Reached end of test";
    end process;
end test;
```


Output:

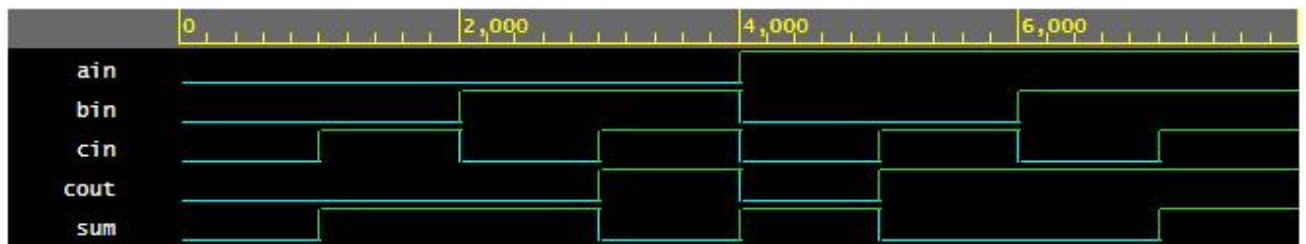

CONCLUSION:

The Full Adder was successfully implemented and simulated in VHDL. All possible input combinations were tested, and the output matched the expected values as per the truth table. This confirms the correct functionality of the Full Adder logic.