

LAB 4

OBJECTIVE: To design and simulate a NAND gate using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

The aim of this lab is to create a NAND gate in VHDL and simulate it using a testbench. The design code describes the logic of the NAND gate, and the testbench applies both possible input combinations to validate the behavior of the gate.

VHDL CODE

DESIGN

```
library ieee;
use ieee.std_logic_1164.all;

entity nandgate is
    port(
        a,b:in std_logic;
        c: out std_logic
    );
end nandgate;
```

```
architecture behavior of nandgate is
    begin
        c <= not (a and b);
    end behavior;
```

TESTBENCH

```
library ieee;
use ieee.std_logic_1164.all;

entity nandgate_testbench is
end nandgate_testbench;

architecture test of nandgate_testbench is
    component nandgate
```

```
    port(
        a,b: in std_logic;
        c: out std_logic
    );
end component;

    signal ak,bk,ck: std_logic;

    begin


        nand_gate: nandgate port map(a=>ak,
        b=>bk, c=>ck);

        process begin

            ak <= '0';bk <= '0';wait for 1 ns;
            ak <= '0';bk <= '1';wait for 1 ns;
            ak <= '1';bk <= '0';wait for 1 ns;
            ak <= '1';bk <= '1';wait for 1 ns;

            assert false report "Completed
            successfully";
            wait;
        end process;
    end test;
```

Output:

 

CONCLUSION:

The NOT gate was successfully simulated. The output matched the expected behavior where ck is the inverse of ak for all input combinations. The use of a simple testbench allowed for effective verification of the circuit behavior in a VHDL simulation environment.