

LAB 5

OBJECTIVE: To design and simulate a **Half Adder Circuit** using VHDL, and verify its functionality using a testbench.

TOOLS USED:

- VHDL (VHSIC Hardware Description Language)
- <https://www.edaplayground.com/> (for simulation)

THEORY:

A Half Adder is a basic combinational circuit that adds two single-bit binary numbers. It produces two outputs:

- Sum (S): XOR of inputs A and B
- Carry (C): AND of inputs A and B

VHDL CODE

DESIGN

```
library ieee;
use ieee.std_logic_1164.all;

entity ha is
    port(
        a: in std_logic;
        b: in std_logic;
        c: out std_logic;
        s: out std_logic);
end ha;
```

```
architecture behave of ha is
begin
    s <= a xor b;
    c <= a and b;
end behave;
```

TESTBENCH

```
library ieee;
use ieee.std_logic_1164.all;

entity ha_testbench is
end ha_testbench;
```

```
architecture test of ha_testbench is
    component ha
        port(a: in std_logic;
             b: in std_logic;
             c: out std_logic;
             s: out std_logic);
    end component;


    signal ain, bin, carry, sum : std_logic;

begin
    half_adder: ha port map (a => ain, b =>
        bin, c => carry, s => sum);

    process begin
        ain <= '0'; bin <= '0'; wait for 1 ns;
        ain <= '0'; bin <= '1'; wait for 1 ns;
        ain <= '1'; bin <= '0'; wait for 1 ns;
        ain <= '1'; bin <= '1'; wait for 1 ns;

        assert false report "Reached end of test";wait;
    end process;
end test;
```

Output:

 

CONCLUSION:

The Half Adder was successfully implemented and simulated in VHDL. The outputs of the simulation matched the expected values based on the truth table of a half adder. The testbench applied all input combinations and validated the behavior effectively.